

N Bit Full adder and Subtractor

T.Priyanka & M.Priyanka

March 8, 2019

Bullet Points

- ▶ Let A and B be two N-bit inputs(which are N input buses, each) and Cin is input carry.
Cin is 0 N-bit addition is performed when its 1 N-bit subtraction is performed.
- ▶ Output consists of N+1 bits i.e N bit sum or difference and 1 bit carry or borrow
- ▶ We can construct a N Bit Full Adder using four 1 Bit Full Adders in a specific way.
- ▶ Lets see how the Truth Table of a 1 Bit Full Adder looks.
- ▶ $S = A.B.Cin + Cout!(A+B+Cin)$
- ▶ $Cout = A.B + B.Cin + Cin.A$

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

{Table 2} : Truth Table of a 1 Bit Full Adder.

- ▶ For a N bit adder we have N bits in the A bus: $A_n, A_{(n-1)}, \dots, A_2, A_1, A_0$ and N bits in the B bus: $B_n, B_{(n-1)}, \dots, B_2, B_1, B_0$.
- ▶ Here, the bits A_n and B_n represent the MSB (Most Significant Bit).
- ▶ The corresponding bits are added, bitwise and if there's Carry generated it's passed on to the next bit where it should be added.
- ▶ Since we are adding only two such numbers, N bits for Sum and one additional bit for Carry-Out would be sufficient.

- ▶ For a N Bit Subtractor, we can obtain the result using 2s complement of B.
- ▶ 2s complement of B would be $B' + 1$. Hence $A - B = A + B' + 1$.
- ▶ Hence by including an XOR gate just before sending the input bits of B to the Full Adder, we can get the operation of Subtraction.
- ▶ The two inputs to the XOR gate would be each individual B bit along with Cin.

The End